

ELEN0037

Microelectronics

Tutorials

Pouyan Ebrahimbabaie, Vinayak Pachkawade, Thomas Schmitz

With special thanks to Vincent Pierlot

University of Liège - Montefiore Institute
EMMI Unit: Electronics, Microsystems, Measurements, and Instrumentation

Tutorial 4: Switched-Capacitor circuits, Filters

Exercise 1 (1st, P10.5/2nd, P14.11)

Find the capacitance values needed for a first order switched-capacitor circuit such that its 3-dB point is at 10 kHz when a clock frequency of 100 kHz is used. Use the bilinear transform. It is also required that the discrete-time zero is at $z = 0$ and that the DC gain be unity. Assume $C_A = 10 \text{ pF}$.¹² What is the gain at $f = 50 \text{ kHz}$?³ The transfer function of a first order switched-capacitor circuit is given by:

$$H(z) = \frac{-\left(\frac{C_1+C_2}{C_A}\right)z + \frac{C_1}{C_A}}{\left(\frac{C_A+C_3}{C_A}\right)z - 1},$$


with a zero at $\frac{C_1}{C_1+C_2}$, and a pole at $\frac{C_A}{C_A+C_3}$.

¹ $H(z) = \frac{0.46673}{z-0.53327}$


² $C_1 = 0$, $C_A = 10 \text{ pF}$, $C_3 = 8.752 \text{ pF}$, $C_2 = -C_3$ (\Rightarrow differential input)

³ $G = |H(-1)| = 0.304 = -10.33 \text{ dB}$

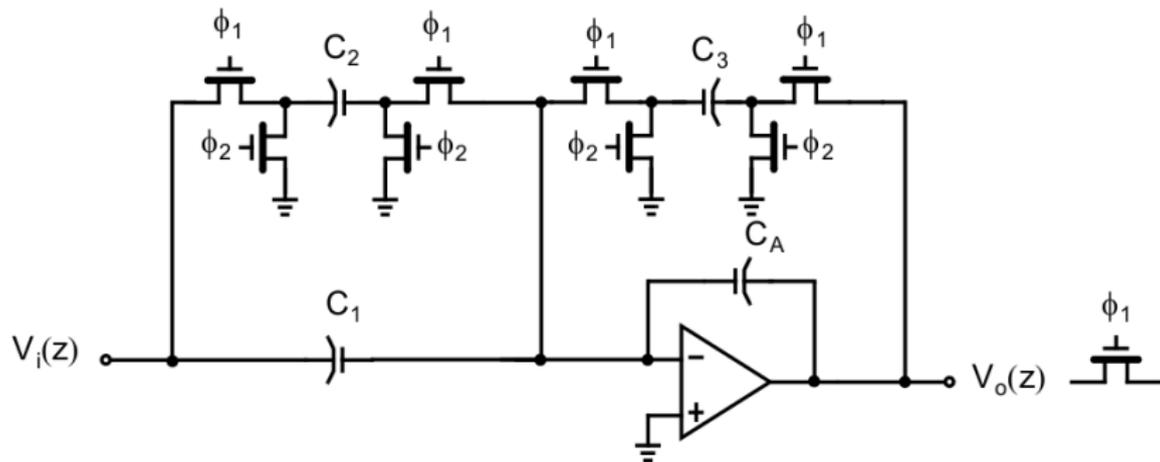Exercise 1 (first order switched-capacitor circuit)



(a)

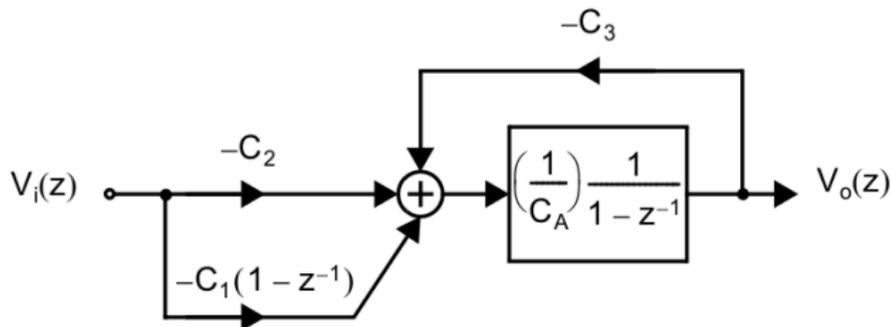

Exercise 2 (first order switched-capacitor circuit)

Based on the previous exercise:

- 1 What is the gain at $f = 10 \text{ kHz}$?⁴
- 2 What would you expect, knowing that $f = f_{3\text{-dB}}$?⁵
- 3 Re-compute the transfer function, by using the exact transform $z = e^{j\omega T}$ in order to find the 3-dB point exactly at 10 kHz .⁶
- 4 What is the real 3-dB frequency in the first approach?⁷
- 5 Derive the discrete-time relationship of this first order switched-capacitor circuit and propose an implementation in a digital system (DSP, μC , FPGA).⁸

⁴ $G = |H(e^{j2\pi \frac{10}{100}})| = 0.719$

⁵ We expect $G = \frac{1}{\sqrt{2}} = 0.707\dots$

⁶ $H(z) = \frac{0.45589}{z - 0.54411}$, ($z_p = \alpha = 2 - \cos(\omega_0 T) - \sqrt{(\cos(\omega_0 T) - 2)^2 - 1}$)

⁷ $f_0 = 10.354 \text{ kHz}$, ($f_0 = \frac{1}{2\pi} f_s \arccos\left(\frac{4\alpha - \alpha^2 - 1}{2\alpha}\right)$)

⁸ $y[k] = \alpha y[k-1] + (1 - \alpha)x[k] = y[k-1] + (1 - \alpha)(x[k] - y[k-1])$

Exercise 3 (1st, P10.6/2nd, P14.12)

Find the capacitance values needed for the same first order switched-capacitor circuit such that its 3-dB frequency is at 1 kHz when a clock frequency of 50 kHz is used. Use the exact transform. It is also required that the discrete-time zero is at $z = 0$ and that the DC gain be unity. Assume $C_A = 50 \text{ pF}$.⁹ What is the gain (in dB) at $f = 25 \text{ kHz}$?¹⁰

⁹ $C_1 = 0$, $C_3 = 14.202 \text{ pF}$, $C_2 = -C_3$ (\Rightarrow differential input)

¹⁰ $G = |H(-1)| = 0.1244 = -9 \text{ dB}$

Exercise 4 (1st, P10.7/2nd, P14.13)

Find the transfer function of the first order switched-capacitor circuit, when $C_1 = 0 \text{ pF}$, $C_2 = 2 \text{ pF}$, $C_3 = 2 \text{ pF}$, and $C_A = 20 \text{ pF}$.¹¹ What is the magnitude and phase of the gain at DC, $f_s/4$, and $f_s/2$?^{12,13} The transfer function is given by (same as before):

$$H(z) = \frac{-\left(\frac{C_1+C_2}{C_A}\right)z + \frac{C_1}{C_A}}{\left(\frac{C_A+C_3}{C_A}\right)z - 1},$$


¹¹ $H(z) = \frac{-0.1z}{1.1z-1}$

¹² $G_{\frac{f_s}{4}} = |H(e^{j\frac{\pi}{2}})| = 0.0673, \angle = 137.73^\circ$

¹³ $G_{\frac{f_s}{2}} = |H(e^{j\pi})| = 0.0476, \angle = 180^\circ$

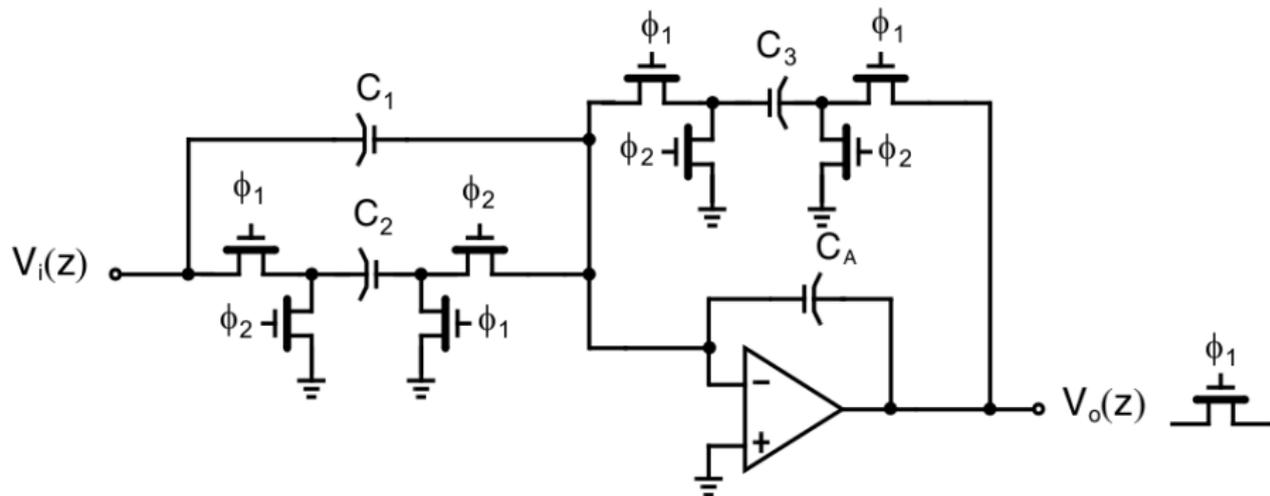Exercise 5 (1st, P10.8/2nd, P14.14)

Show that the transfer function of the following SC circuit




is given by:


$$H(z) = \frac{-\left(\frac{C_1}{C_A}\right)z + \frac{C_1+C_2}{C_A}}{\left(\frac{C_A+C_3}{C_A}\right)z - 1}.$$

Use the signal-flow-graph analysis. Compare this transfer function to the one used previously.

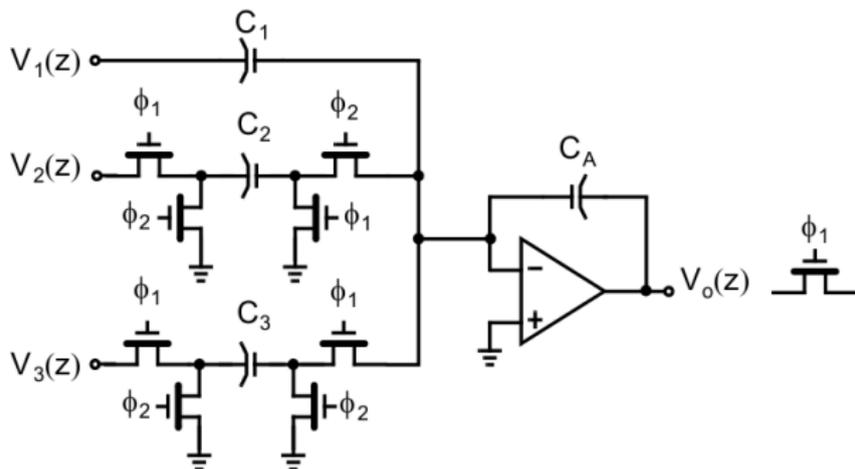Exercise 5 (Signal-Flow-Graph Analysis review)



(a)

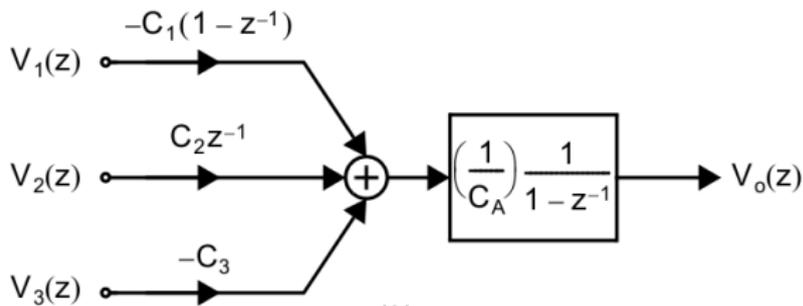

(b)

Exercise 6 (1st, P10.9/2nd, P14.16)

Show that when $K_6 = 0$ in the low-Q switched-capacitor biquad circuit, if the poles are complex, they lie precisely on the unit circle (i.e. the circuit is a resonator).¹⁴ The transfer function of the low-Q SC biquad is given by:

$$H(z) = -\frac{(K_2 + K_3)z^2 + (K_1K_5 - K_2 - 2K_3)z + K_3}{(1 + K_6)z^2 + (K_4K_5 - K_6 - 2)z + 1}.$$

¹⁴ $K_6 = 0 \Rightarrow D(z) = z^2 + (K_4K_5 - 2)z + 1 \Rightarrow z_1z_2 = 1, z_2 = z_1^* \Rightarrow |z_1| = 1$